

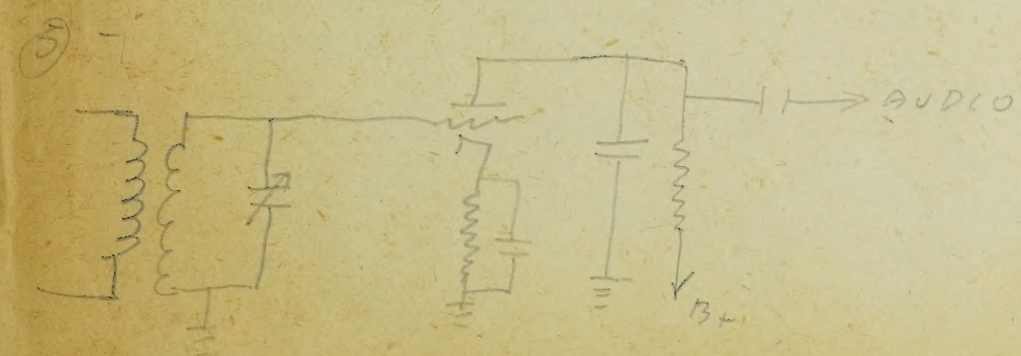
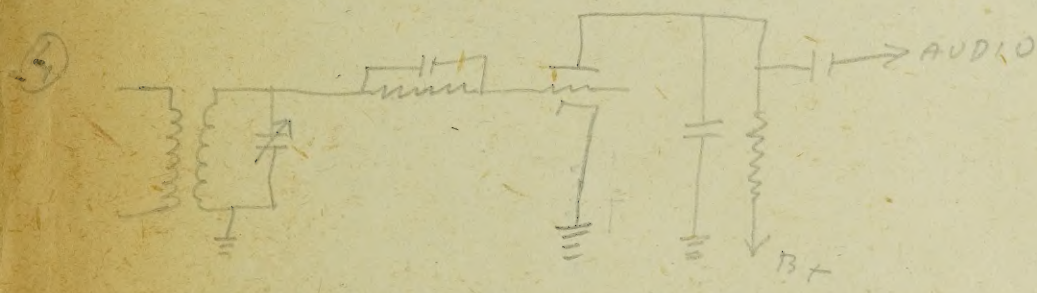
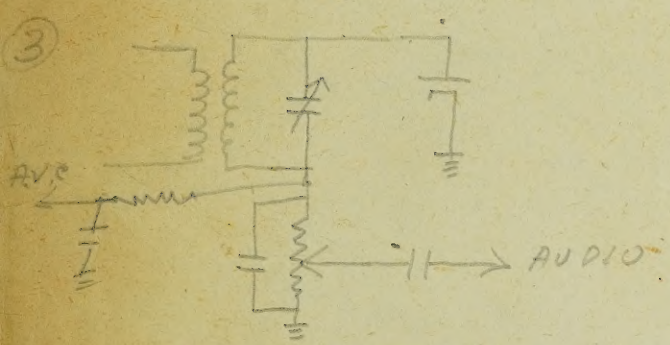
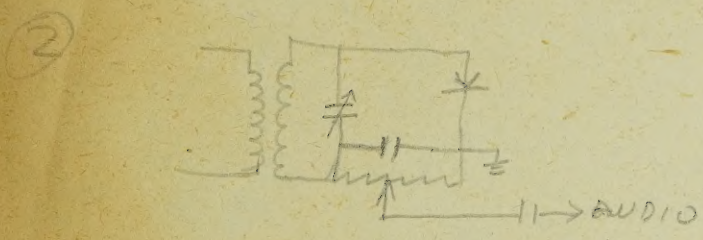
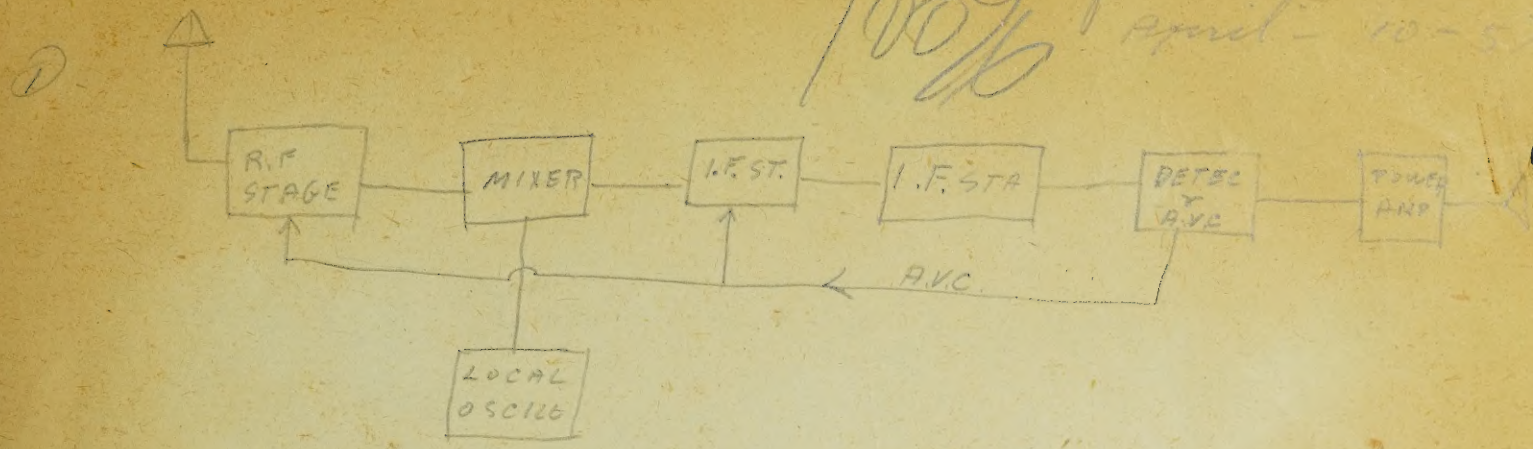
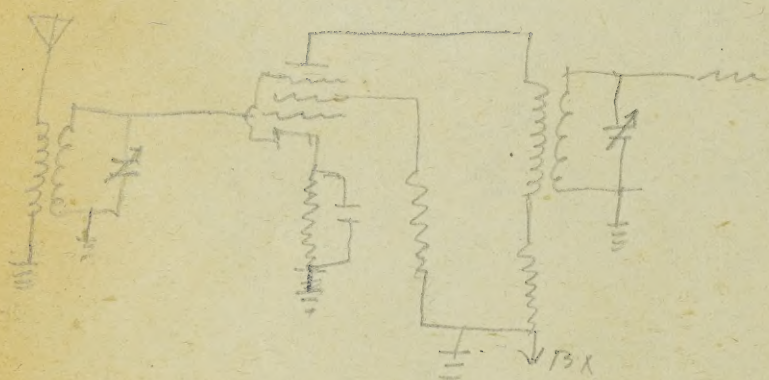


100% *Quartz circuit*
April - 10 - 57

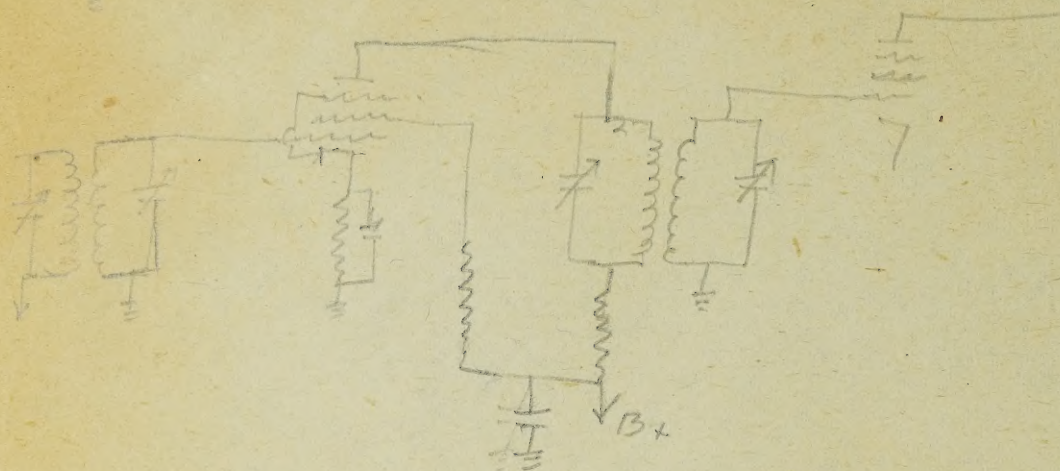

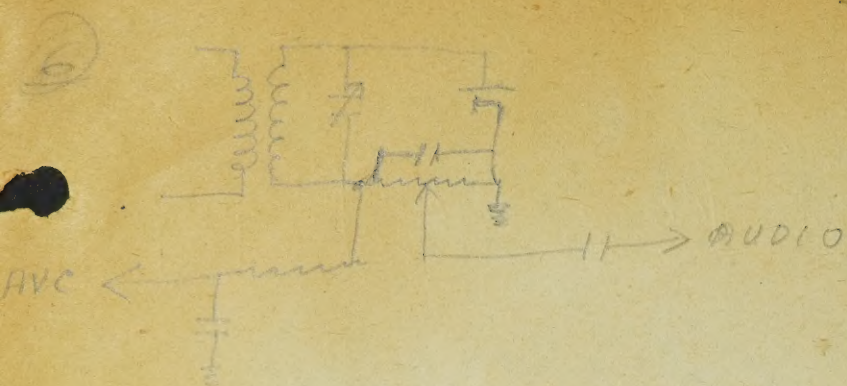

- ① WITH AN A.C. VOLTMETER ACROSS THE OUTPUT TRANSFORMER.
 - ② WITH THE SCOPE CONNECTED TO THE AUDIO OUTPUT OF THE DETECTOR.
 - ③ A NEGATIVE D.C. VOLTMETER CONNECTED TO THE A.V.C.
- ④ AN IMAGE FR. IS AN UNDESIRABLE FR. WHICH BEATS WITH THE LOCAL OSCILLATOR FR. TO PRODUCE THE I.F. FR. IT CAN BE ABOVE OR BELOW THE OSCILLATOR FR. BY THE AMOUNT OF THE I.F. FR.